

scientific
analog

Putting It All Together: CTLE Modeling Example

Scientific Analog, Inc.


July 2017

Modeling Example: CTLE

- Continuous-time linear equalizer (CTLE) is a key building block in wireline receivers
 - Intent is a linear filter but can be nonlinear (e.g. gain compression)
- Three different ways to model CTLEs with *XMODEL*:
 - Block-level model using function primitives
 - Circuit-level model calibrated using *MODELFIT*
 - Circuit-level model generated using *MODELZEN*

 Example CTLE

- CTLE with capacitive source degeneration




- AC transfer function $H(s)$ has two poles & one zero:

$$H(s) = A_{DC} \frac{1 + s/z_1}{(1 + s/p_1)(1 + s/p_2)}$$

- Each output swing is limited to $V_{DD} - I_B R_L \sim V_{DD}$
- Tunable by adjusting R_C and C_C
- ***ctl_model:ctl_core:schematic***

CTLE Block-Level Model

 - Model a CTLE stage with
 - Large-signal DC characteristics
 - Small-signal AC characteristics



Hammerstein Model

Exercise #1: Model Fitting


- Example is located in *ctle_model/ctle_func*
 - Model template: *ctle_func.sv.empty*
 - Model fitting script: *fit_ctle.py*
- First, generate netlist for the following two cellviews (i.e. click *GLISTER*->*Generate Netlist* in Virtuoso):
 - *ctle_model:ctle_basic:schematic*
 - *ctle_model:ctle_core:schematic*
- Second, fit the model parameters by executing:

```
$ cd $TUTORIAL_HOME/ctle_model/ctle_func  
$ make
```

Model Extraction with *MODELFIT*


- *MODELFIT* extracts parameters for model templates chosen for DC and AC characteristics

DC Characteristics

 

`modelfit("pwl_func")`

AC Characteristics

 

`modelfit("filter")`

Exercise #1: Simulation

- Run DC simulation with slowly increasing input:

```
$ cd $TUTORIAL_HOME/ctle_model/ctle_func/tb/dc  
$ make
```

- Run transient simulation with PRBS data input:

```
$ cd $TUTORIAL_HOME/ctle_model/ctle_func/tb/prbs  
$ make
```

XMODEL-SPICE Cosimulation

- Command-line method to run *XMODEL*-SPICE cosimulation (e.g. VCS + XA):


```
xmodel <source files> --top <top modulename>  
    --simulator vcs --spice xa --cosimctrl vcsAD.init
```

- vcsAD.init is the cosimulation control file:


```
use_spice -cell ctle_basic;  
choose xa tb_ctle.sp -c xa_config;
```


CTLE Simulation Results

DC transfer

 


PRBS response

 

Circuit-Level Modeling of CTLE

- If modeling $H(s)$ is the only requirement, using the *filter* primitive would be the easiest
- Considering the requirements on adaptability and nonlinearity, it'd be easier to use *circuit-level models*
- Circuit-level modeling (CLM) allows you to describe circuits directly with circuit-level components
 - e.g. transistors, resistors, capacitors, ...
 - *XMODEL* extracts $H(s)$ at run-time
 - Can easily model tunable R and C and signal clipping

11

 


CTLE Model Parameters

- Behavioral parameters
 - **gain**: small-signal DC gain (A_{DC})
 - **pole1**: lower pole frequency (real-valued; p_1)
 - **pole2**: higher pole frequency (real-valued; p_2)
 - **zero**: zero frequency (real-valued; z)
 - **itotal**: current consumption ($\sim 1/\text{output resistance}$)
 - **vout_max**: maximum output voltage ($=V_{dd}$)
 - **vout_min**: minimum output voltage
 - **vic_max**: maximum input common-mode voltage
- Circuit parameters
 - $g_m, V_{th}, R_L, C_L, R_C, C_C, I_B, V_{DD}$

AC small-signal param.'s

DC large-signal param.'s

CTLE Circuit Analysis

 

- AC small-signal param.'s:

$$A_{DC} = \frac{g_m R_L}{1 + g_m R_C / 2}$$

$$p_1 = (1 + g_m R_C / 2) / R_C C_C$$

$$p_2 = 1 / R_L C_L$$

$$z = 1 / R_C C_C$$

- DC large-signal param.'s:

$$V_{DD} - I_B R_L \leq V_{out} \leq V_{DD}$$

$$V_{in,cm} \leq V_{out,cm} + V_{th}$$

$$= V_{DD} - I_B R_L / 2 + V_{th}$$

Parameter Definitions

```

module ctle_basic (
    `input_xreal inp, inn,          // input signals
    `output_xreal outp, outn        // output signals
);

// behavioral parameters
parameter real gain = 2;           // small-signal DC gain
parameter real pole1 = 0.5e9;      // lower pole frequency (in Hz)
parameter real pole2 = 10e9;       // higher pole frequency (in Hz)
parameter real zero = 0.1e9;       // zero frequency (in Hz)
parameter real itotal = 1e-3;      // total current consumption
parameter real vout_max = 1.2;     // maximum output voltage (=Vdd)
parameter real vout_min = 0.8;     // minimum output voltage
parameter real vic_max = 1.0;      // maximum input common-mode voltage


// circuit parameters
parameter real Vdd = vout_max;     // supply voltage
parameter real Ib = itotal;        // bias current
parameter real Vth = vic_max - (vout_max + vout_min) / 2; // threshold voltage
parameter real Rload = (vout_max - vout_min) / Ib;        // load resistance
parameter real Cload = 1.0 / (Rload * 2 * M_PI * pole2);  // load capacitance
parameter real Gm = gain / Rload * (pole1 / zero);        // transconductance
parameter real Rc = (pole1 / zero - 1) * 2 / Gm;          // source-degeneration resistance
parameter real Cc = 1.0 / (Rc * 2 * M_PI * zero);        // source-degeneration capacitance

...

```


15

 - A circuit schematic based on PTM 45nm library
- You can write a model fitting script in Python using *XMULAN* and *MODELFIT*



Parameter Extraction from Circuit (2)

 - Script *fit_ctle.py* performs three simulations to extract the parameters
 - DC simulation to extract *vic_max*, *itotal* parameter
 - DC simulation to extract *vout_min*
 - AC simulation to extract *gain*, *pole1*, *pole2*, *zero*



Exercise #2: Model Fitting

- Example is located in *ctle_model/ctle_clm*
 - Model template: *ctle_clm.sv.empty*
 - Model fitting script: *fit_ctle.py*
- Fit the model parameters and generate a model by executing:

```
$ cd $TUTORIAL_HOME/ctle_model/ctle_clm  
$ make
```

Exercise #2: Simulation

- Run DC simulation with slowly increasing input:


```
$ cd $TUTORIAL_HOME/ctlc_model/ctlc_clm/tb/dc  
$ make
```

- Run transient simulation with PRBS data input:

```
$ cd $TUTORIAL_HOME/ctlc_model/ctlc_clm/tb/prbs  
$ make
```


Simulation Results (1)

- DC gain compression effect

 

Simulation Results (2)

- Comparison of waveforms w/ PRBS input

 

Model Generation with *MODELZEN*

- ***MODELZEN*** can automatically generate structural models from SPICE netlists
 - Useful for bottom-up modeling of complex analog circuits
 - Individual device parameters are calibrated via SPICE sim.
 - The extracted models also simulate in an event-driven way.



Exercise #3: Model Generation

- Example is located in *ctle_model/ctle_mzen*
 - Technology configuration file: *tech_config.py*
- Generate a model by executing:

```
$ cd $TUTORIAL_HOME/ctle_model/ctle_mzen  
$ modelzen -c tech_config.py ctle_core.sp -o ctle_mzen.sv
```

Or, simply:

```
$ cd $TUTORIAL_HOME/ctle_model/ctle_mzen  
$ make
```

Exercise #3: Simulation

- Run DC simulation with slowly increasing input:


```
$ cd $TUTORIAL_HOME/ctle_model/ctle_mzen/tb/dc  
$ make
```

- Run transient simulation with PRBS data input:


```
$ cd $TUTORIAL_HOME/ctle_model/ctle_mzen/tb/prbs  
$ make
```

CTLE Simulation Results

DC transfer

 


PRBS response

 

 Exercise #5: Cosimulation Netlisting

- Generate cosimulation netlist using *GLISTER*
- *ctle_model:trx_ctle_basic: config*



Virtuoso® Hierarchy Editor: (ctle_model:trx_ctle_basic config)

cadence

File Edit View Plugins Help

Top Cell

Library: ctle_model

Cell: trx_ctle_basic

View: schematic

Open Edit

Global Bindings

Library List: ctle_model

View List: xl_sch schematic config

Stop List: spiceD spectre veriloga

Constraint List:

Table View Tree View

Cell Bindings

Library	Cell	View Found	View To Use	Inherited View List
analogLib	cap	hspiceD		xmodel verilog func...
analogLib	idc	hspiceD		xmodel verilog func...
analogLib	nmos	hspiceD		xmodel verilog func...
analogLib	res	hspiceD		xmodel verilog func...
analogLib	vdc	hspiceD		xmodel verilog func...
ctle_model	channel	schematic		xmodel verilog func...
ctle_model	ctle_basic	schematic	schematic	xmodel verilog func...
ctle_model	ctle_bias_sp	schematic		xmodel verilog func...
ctle_model	ctle_core	schematic		xmodel verilog func...
ctle_model	trx_ctle_basic	schematic	schematic	xmodel verilog func...
xmodel_prims	add	xmodel		xmodel verilog func...
xmodel_prims	clk_gen	xmodel		xmodel verilog func...
xmodel_prims	cmos	xmodel		xmodel verilog func...
xmodel_prims	filter	xmodel		xmodel verilog func...
xmodel_prims	prbs_gen	xmodel		xmodel verilog func...
xmodel_prims	transition	xmodel		xmodel verilog func...


Choose schematic

Namespace: CDBA Filters: OFF


6(8) >

 Exercise #5: Cosimulation Testbench

- Choose the simulator and config view for cosimulation
 - VCS-XA setup is in: *ctle_model:trx_ctle_basic:tb_vcs*



Choose Simulator

 

Choose Config View
Defining the Hierarchy


Exercise #5: Cosimulation Setup

- You can generate netlists and run simulation using the same interface of Testbench Editor

SPICE Solver →



Top-Level SPICE Input File →

Co-simulation Control File →

 

  Exercise #5: Cosimulation Setup (2)

- NCVerilog-Spectre cosimulation setup is found in:
ctle_model:trx_ctle_basic:tb_ncverilog



Summary

- ***XMODEL*** is a fast analog/mixed-signal simulator that works seamlessly with digital verification flows (SystemVerilog, UVM, ...)
 - Achieves both speed and accuracy ($\Leftrightarrow$ Verilog-A, RNV)
 - Supports both block- and circuit-level models ($\Leftrightarrow$ RNV)
- ***GLISTER***, ***MODELZEN***, and ***MODELFIT*** are convenient tools that help you compose analog models and verify them against SPICE